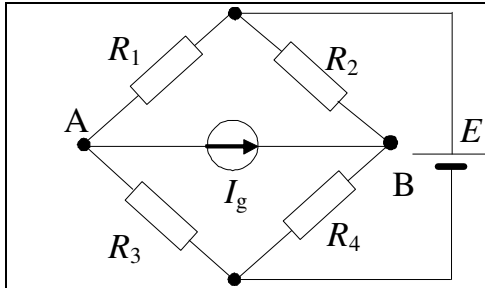



1. Vrednosti elemenata u kolu na slici 1 su:

$$R_1=R_2=800 \Omega, R_3=600 \Omega, R_4=400 \Omega, I_g=20 \text{ mA}, E=10 \text{ V}$$


Primenom Tevenenove teoreme odrediti ekvivalentni Tevenenov generator kojim se može zameniti ovo kolo između tačaka A i B.



slika 1

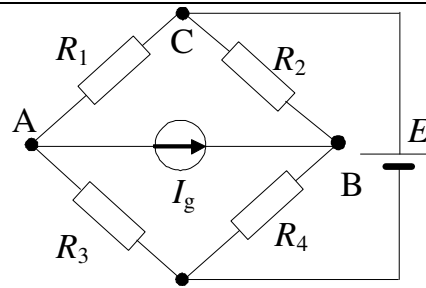

slika 1-1

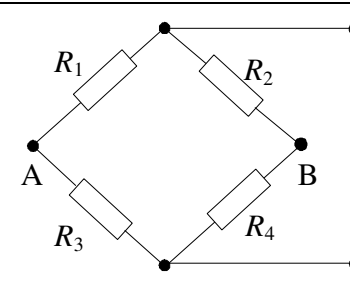

slika 1-2

$$\begin{aligned} n_g &= 6 \\ n_c &= 4 \\ n_{ks} &= 6 - (4 - 1) = 3 \rightarrow 2(I_g) \\ n_{n\check{c}} &= 4 - 1 = 3 \rightarrow 2(E) \end{aligned}$$

$$V_C = E = 10 \text{ V}$$

$$\left(\frac{1}{R_1} + \frac{1}{R_3}\right) \cdot V_A - \frac{1}{R_1} V_C = -I_g$$

$$\left(\frac{1}{R_2} + \frac{1}{R_4}\right) \cdot V_B - \frac{1}{R_2} V_C = I_g$$

$$V_A = -2,57 \text{ V}$$

$$V_B = 8,67 \text{ V}$$

$$E_T = U_{AB} = V_A - V_B = -11,24 \text{ V}$$








$$\begin{aligned} R_T &= R_1 \parallel R_3 + R_2 \parallel R_4 \\ R_T &= 609 \Omega \end{aligned}$$

2. Za kolo dato na slici 2 su poznate sledeće vrednosti elemenata: $E=12\text{ V}$, $R_1=60\ \Omega$, $R_2=40\ \Omega$, $L=20\text{ mH}$
 Kolo se nalazi u stacionarnom režimu sa otvorenim prekidačem P. U trenutku $t_0=0$ zatvori se prekidač.

a) Odrediti vrednost napona na zavojnici u $t_1=2\text{ ms}$.

b) Nacrtati dijagrame napona na zavojnici i struje kroz zavojnicu.



c) U trenutku $t_2=3\text{ ms}$ greškom dolazi do kratkog spoja krajeva otpornika R_2 . Nacrtati promene na dijagramima napona i struje zavojnice koje nastaju u t_2 .
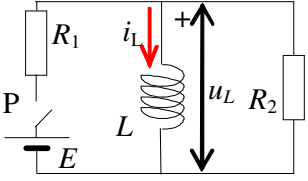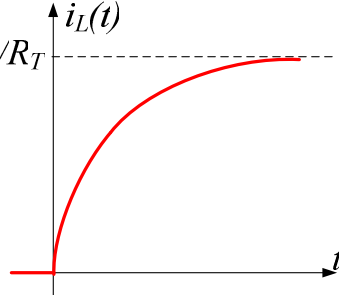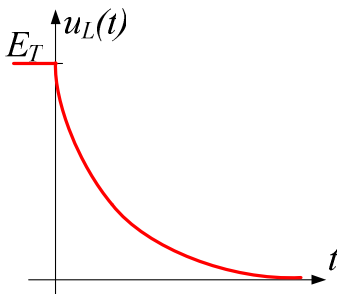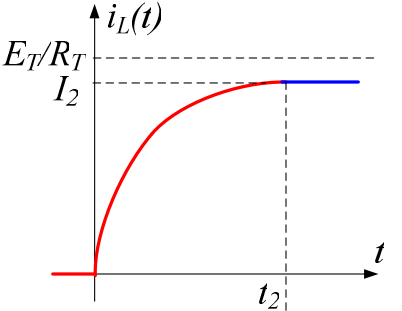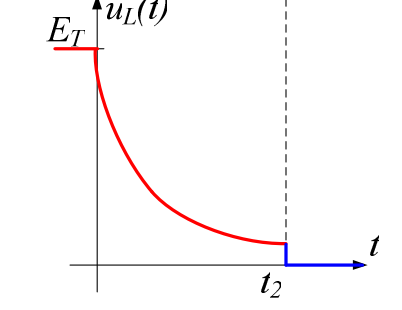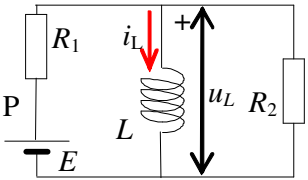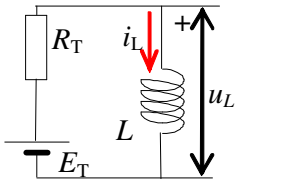
<p>a) Stacionarno stanje:</p>  <p>$i_L(t=0^-) = 0$ $u_L(t=0^-) = 0$</p>	$E_T = R_T \cdot i_L + u_L$ $u_L = L \cdot \frac{di_L}{dt}$ $i_L = i_{Lp} + i_{Lh}$ $i_{Lp} = \frac{E_T}{R_T}$ $i_{Lh} : R_T \cdot i_L + L \cdot \frac{di_L}{dt} = 0$ $i_{Lh} = K \cdot e^{-\frac{R_T}{L}t}$ $i_L = \frac{E_T}{R_T} + K \cdot e^{-\frac{R_T}{L}t}$	<p>b)</p>  	<p>c)</p>  
<p>Zatvoren prekidač:</p>  $E_T = E \cdot \frac{R_2}{R_1 + R_2} = 4,8\text{ V}$ $R_T = \frac{R_1 \cdot R_2}{R_1 + R_2} = 24\ \Omega$ 	$i_L(t=0^-) = i_L(t=0^+) \Rightarrow K = -\frac{E_T}{R_T}$ $i_L(t) = \frac{E_T}{R_T} \cdot \left(1 - e^{-\frac{R_T}{L}t}\right)$ $u_L(t) = E_T \cdot e^{-\frac{R_T}{L}t}$ $u_L(0^+) = U_0 = E_T = 4,8\text{ V}$ $u_L(t_1^-) = 0,44\text{ V}$ $i_L(t_1^-) = 0,18\text{ A} = I_1$	<p>Kratak spoj krajeva otpornika R_2:</p> $t \geq t_2$ $u_L(t) = 0$ $L \cdot \frac{di_L}{dt} = 0 \Rightarrow i_L(t) = K$ $i_L(t_2^-) = i_L(t_2^+) = I_2$ $i_L(t) = I_2$	

3. Za kolo prikazano na slici 3 poznato je: $u(t)=6\sin(10^3t-\pi/3)$ V i $i(t)=3\cos(10^3t-\pi/3)$ mA

a) Odrediti vrednost elementa kojim se može zameniti admitansa \underline{Y} .

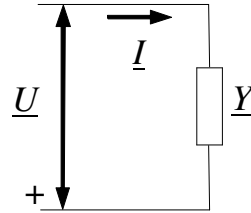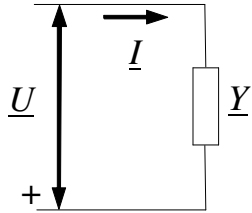b) Odrediti kompleksnu snagu koja se razvija na admitansi \underline{Y} .



a)

$$u(t) = 6 \cdot \cos\left(\frac{\pi}{2} - 10^3 \cdot t + \frac{\pi}{3}\right) \text{ V}$$

$$u(t) = 6 \cdot \cos\left(-10^3 \cdot t + \frac{5 \cdot \pi}{6}\right) \text{ V}$$

$$u(t) = 6 \cdot \cos\left(10^3 \cdot t - \frac{5 \cdot \pi}{6}\right) \text{ V}$$

$$\underline{U} = \frac{6}{\sqrt{2}} \cdot e^{-j \frac{5 \cdot \pi}{6}} \text{ V}$$

$$\underline{I} = \frac{3}{\sqrt{2}} \cdot e^{-j \frac{\pi}{3}} \text{ mA}$$

$$\underline{Y} = -\frac{I}{U} = -0,5 \cdot e^{j \frac{\pi}{2}} \text{ mS}$$

$$\underline{Y} = 0,5 \cdot e^{-j \frac{\pi}{2}} \text{ mS}$$

$B < 0 \Rightarrow$ zavojnica

$$\frac{1}{\omega \cdot L} = 0,5 \text{ mS}$$

$$L = 2 \text{ H}$$

b)

$$\underline{S} = -\underline{U} \cdot \underline{I}^*$$

$$\underline{S} = 9 \cdot e^{j \frac{\pi}{2}} \text{ mVA}$$

4. Pretežno kapacitivni trofazni prijemnik vezan u trougao priključen je na simetričan trofazni sistem linijskog napona mreže 380 V i učestanosti 50 Hz. Faktor snage prijemnika je $\cos \varphi = 0,75$. Efektivna vrednost linijske struje iznosi $I_l = 15$ A.

- Odrediti aktivnu i reaktivnu snagu prijemnika.
- Naći vrednost otpornosti i kapacitivnosti po fazi prijemnika.
- Nacrtati fazorski dijagram faznih napona i struja.

a)

$$U_f = U_l = 380 \text{ V}$$

$$I_f = \frac{I_l}{\sqrt{3}} = 8,66 \text{ A}$$

$$P = 3 \cdot U_f \cdot I_f \cdot \cos \varphi$$

$$P = 7404 \text{ W}$$

$$\sin \varphi = -\sqrt{1 - \cos^2 \varphi} = -0,66$$

$$Q = 3 \cdot U_f \cdot I_f \cdot \sin \varphi$$

$$Q = -6515 \text{ VA}_r$$

b)

$$Z = \frac{U_f}{I_f} = 43,88 \Omega$$

$$R = Z \cdot \cos \varphi = 32,9 \Omega$$

$$-\frac{1}{\omega \cdot C} = Z \cdot \sin \varphi \Rightarrow C = -\frac{1}{\omega \cdot Z \cdot \sin \varphi} = 0,11 \text{ mF}$$

c)

$$\varphi = -41,3^\circ$$

